I2CA Homework 6 Dimitri Tabatadze

## Proof.

Given

$$d(1) = d(FA)$$
  
$$d(n) = d(n/2) + d(MUX)$$

assume

$$d(n) = d(FA) + d(MUX) \cdot \log_2 n$$

base case:

1.

 $d(1) = d(FA) + d(MUX) \cdot \log_2(1)$  $= d(FA) + 3 \cdot 0$ = d(FA)

induction step:

$$\begin{split} d(n) &= d(n/2) + d(\text{MUX}) \\ &= d(\text{FA}) + d(\text{MUX}) \cdot \log_2(n/2) + d(\text{MUX}) \\ &= d(\text{FA}) + d(\text{MUX}) \cdot (\log_2 n - 1) + d(\text{MUX}) \\ &= d(\text{FA}) + d(\text{MUX}) \cdot \log_2 n \\ &= d(\text{FA}) + 3 \cdot \log_2(n) \end{split}$$

proven.

## 2. Given

$$d(2) = 1,$$
  

$$d(n) = d(n/2) + 2,$$
  

$$c(2) = 1,$$
  

$$c(n) \le c(n/2) + n$$

## Proof.

assume  $d(n) = 2 \cdot \log_2 n - 1$  base case:

$$d(2) = 2 \cdot \log_2 2 - 1$$
  
=  $2 \cdot 1 - 1$   
= 1

induction step:

$$\begin{split} d(n) &= d(n/2) + 2 \\ &= 2 \cdot \log_2(n/2) - 1 + 2 \\ &= 2 \cdot (\log_2 n - 1) + 1 \\ &= 2 \cdot \log_2 n - 2 + 1 \\ &= 2 \cdot \log_2 n - 1 \end{split}$$

$$d(n) = 2 \cdot \log_2 n - 1 = O(\log n)$$

proven.

I2CA Homework 6 Dimitri Tabatadze

## Proof.

assume  $c(n) \leq 2n$  base case:

$$c(2) = 1 \leq 4$$

induction step:

$$\begin{split} c(n) & \leq c(n/2) + n \\ & \leq (n/2) \cdot 2 + n \\ & \leq 2n \end{split}$$

$$c(n) \le 2n = O(n)$$

proven.

3. :(

4.

$$ovf u = (sub \wedge (\langle a \rangle < \langle b \rangle)) \vee (\overline{sub} \wedge C_n) \wedge u 
= ((sub \wedge \overline{C_n}) \vee (\overline{sub} \wedge C_n)) \wedge u 
= (sub \oplus C_n) \wedge u$$

5. Given  $a_{n-1} \oplus b_{n-1} \oplus c_{n-1} = S_{n-1}$  we can simply say that  $c_{n-1} = a_{n-1} \oplus b_{n-1} \oplus S_{n-1}$ 

6. :(