CA Lab: Lab 5

student: Dimitri Tabatadze

April 6, 2023

Task Description

- 1. In the module file use always statement with case. (20 points)
- 2. Write the testbench. (20 points)
- 3. Use RTL viewer and show the drawing of 2-t0-4 decoder. (5 points)
- 4. Simulate the testbench and make the analyze of timing diagram. (10 points)
- 5. Run the code on the board. (40 points)

Solution

1. The code:

```
module decoder (
   input [1:0] in,
   output reg [3:0] out);

always @ (in)
begin
   case (in)
    2'b00 : out = 4'b0001;
   2'b01 : out = 4'b010;
   2'b10 : out = 4'b0100;
   2'b11 : out = 4'b1000;
endcase
end


end
end
end
```

As you see, I have ommitted the default case, which is optional. In this case, the cases are exhaustive, so there's no point to having a default case — it will never be entered.

2. The code:


```
include "decoder.v"
3 module decoder_tb();
5 reg [1:0] in;
6 wire [3:0] out;
  decoder UUT(.in(in), .out(out));
10 initial begin
                                      // These two lines are
11
      $dumpfile("decoder_tb.vcd"); // used for logging
12
                                      // the data, quartus
      $dumpvars(0, decoder_tb);
13
                                      // doesn't need them.
      in = 2'b00;
16
      #100;
      in = 2'b01;
17
      #100;
18
19
      in = 2'b10;
      #100;
20
21
      in = 2'b11;
      #100;
22
23 end
24
25 endmodule
```

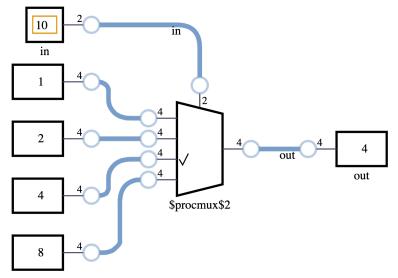3. I don't have quartus, but this is something that should be equivalent to what the RTL viewer would produce. I've give the schematic a test input of 01



This visualization was made using DigitalJS plugin for VSCodium.

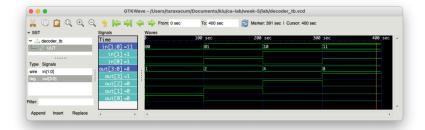 $4.\,$ I used ${\tt vvp}$ for simulation and ${\tt GTKWave}$ for visualization. Here's the result:



It's clear that the program is doing just what we wanted it to do. Given input 11 (which is 3 in decimal), the 3-rd bit (counting from 0) is set, while others are not.

Conclusion

Since I don't have the ability to run Quartus on my laptop and am using FOSS alternatives for doing everything I would have done with quartus, other than being able to run my code on physical hardware, I will be using a friend's laptop (or any laptop I can get a hold of which has quartus installed) to run my code on a board.

Reference

- Where I learned about the always block
- Where I learned about the case statement